

Code No: 153AT

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B. Tech II Year I Semester Examinations, August/September - 2022****ELECTRONIC DEVICES AND CIRCUITS**

(Common to ECE, EIE, MCT)

Time: 3 Hours**Max.Marks:75**

Answer any five questions
All questions carry equal marks

- - -

- 1.a) Derive the expression for diffusion capacitance of a diode.
- b) Discuss how a diode could be used as switch and define all switching times. [8+7]
- 2.a) Derive ripple factor for a bridge rectifier.
- b) Derive expressions for ripple factor of a Full Wave Rectifier with and without a capacitive filter. [8+7]
- 3.a) Determine I_C , I_E and α for a transistor circuit having $I_B=15\mu A$ and $\beta=150$.
- b) Draw and explain the working principle of CE characteristics of a transistor. [8+7]
- 4.a) Find the Q-point of self-bias transistor circuit with the following specifications:
 $V_{CC} = 22.5V$, $R_L = 5.6k\Omega$, $R_C = 1k\Omega$, $R_1 = 90k\Omega$, $R_2 = 10k\Omega$, $V_{BE} = 0.7V$ and $\beta = 55$.
Assume $I_B \gg I_{CO}$.
- b) The reverse leakage current of the transistor when in CB configuration is $0.3 \mu A$ while it is $16 \mu A$ when the same transistor is connected in CE configuration. Determine α , β and γ . [8+7]
- 5.a) Differentiate between a BJT and FET.
- b) Explain the operation of FET with its characteristics and explain the different regions in transfer characteristics. [7+8]
- 6.a) Draw the symbol and equivalent circuit of a UJT. Explain the operation of UJT with the help of its $V - I$ characteristics.
- b) With neat sketches explain about the regulation characteristics of Zener diode. [8+7]
- 7.a) For a CE amplifier given $I_E = 2.5mA$, $h_{fe} = 140$, $h_{oe} = 20\mu s$ and $h_{ob} = 0.5\mu s$. Draw hybrid equivalent circuit.
- b) Compare the three transistor amplifier configurations with related to A_i , A_v , R_i and R_o . [8+7]
- 8.a) With neat sketches, necessary equations explain the drain and transfer characteristics of MOSFET in depletion mode.
- b) Draw the small-signal model of common drain JFET amplifier. Derive expressions for voltage gain and output resistance. [8+7]