

## Multiple Choice Questions & Answers

### 1. What are the basic electrical circuit elements?

- a) Resistors
- b) Inductors
- c) Capacitors
- d) Voltage Sources

Answer: A. Resistors

### 2. Which theorem allows the simplification of complex circuits by replacing a portion with a single equivalent source?

- a) Superposition
- b) Thevenin
- c) Norton
- d) Kirchhoff's Laws

Answer: B. Thevenin

### 3. What is the application of Kirchhoff's Current Law (KCL)?

- a) Voltage
- b) Current
- c) Resistance
- d) Inductance

Answer: B. Current

### 4. How do you analyze a circuit using Kirchhoff's Voltage Law (KVL)?

- a) Voltage
- b) Current
- c) Resistance
- d) Inductance

Answer: A. Voltage

**5. What is the purpose of using Thevenin's Theorem in circuit analysis?**

- a) To simplify
- b) To complicate
- c) To confuse
- d) To obfuscate

Answer: A. To simplify

**6. How does Norton's Theorem differ from Thevenin's Theorem?**

- a) Voltage Source
- b) Current Source
- c) Resistance
- d) Inductance

Answer: B. Current Source

**7. In a first-order RC circuit, what component determines the time constant?**

- a) Resistor
- b) Capacitor
- c) Inductor
- d) Voltage Source

Answer: B. Capacitor

**8. What does the time constant represent in a first-order RL circuit?**

- a) Resistance
- b) Capacitance
- c) Inductance
- d) Voltage

Answer: C. Inductance

**9. How is the Superposition Theorem applied in circuit analysis?**

- a) By considering

- b) By ignoring
- c) By complicating
- d) By simplifying

Answer: A. By considering

**10. What is the primary objective of analyzing circuits using KCL and KVL?**

- a) To confuse
- b) To complicate
- c) To simplify
- d) To obfuscate

Answer: C. To simplify

**11. How do you calculate the equivalent resistance in a circuit using Thevenin's Theorem?**

- a) Open Circuit
- b) Short Circuit
- c) Voltage Source
- d) Current Source

Answer: A. Open Circuit

**12. What is the significance of Norton's Theorem in circuit analysis?**

- a) It simplifies
- b) It complicates
- c) It confuses
- d) It obfuscates

Answer: A. It simplifies

**13. How do you determine the Thevenin equivalent voltage of a circuit?**

- a) By shorting
- b) By opening

- c) By removing
- d) By replacing

Answer: A. By shorting

**14. What is the purpose of using Thevenin's Theorem in circuit analysis?**

- a) To confuse
- b) To complicate
- c) To simplify
- d) To obfuscate

Answer: C. To simplify

**15. How does Superposition Theorem simplify circuit analysis?**

- a) By considering
- b) By ignoring
- c) By complicating
- d) By simplifying

Answer: D. By simplifying

**16. In a first-order RL circuit, what component determines the time constant?**

- a) Resistor
- b) Capacitor
- c) Inductor
- d) Voltage Source

Answer: A. Resistor

**17. How do you calculate the time constant of a first-order RC circuit?**

- a)  $\tau = RC$
- b)  $\tau = LR$
- c)  $\tau = 1/L$
- d)  $\tau = 1/RC$

Answer: A.  $\tau = RC$

**18. What is the purpose of Norton's Theorem in circuit analysis?**

- a) To simplify
- b) To confuse
- c) To complicate
- d) To obfuscate

Answer: A. To simplify

**19. How is Superposition Theorem applied in circuit analysis?**

- a) By considering
- b) By ignoring
- c) By complicating
- d) By simplifying

Answer: B. By ignoring

**20. What is the primary objective of analyzing circuits using KCL and KVL?**

- a) To simplify
- b) To complicate
- c) To confuse
- d) To obfuscate

Answer: A. To simplify

**21. How do you calculate the equivalent resistance in a circuit using Thevenin's Theorem?**

- a) By shorting
- b) By opening
- c) By removing
- d) By replacing

Answer: B. By opening

**22. What is the significance of Norton's Theorem in circuit analysis?**

- a) It simplifies
- b) It complicates
- c) It confuses
- d) It obfuscates

Answer: A. It simplifies

**23. How do you determine the Thevenin equivalent voltage of a circuit?**

- a) By shorting
- b) By opening
- c) By removing
- d) By replacing

Answer: B. By opening

**24. What is the purpose of using Thevenin's Theorem in circuit analysis?**

- a) To simplify
- b) To complicate
- c) To confuse
- d) To obfuscate

Answer: A. To simplify

**25. How does Superposition Theorem simplify circuit analysis?**

- a) By considering
- b) By ignoring
- c) By complicating
- d) By simplifying

Answer: D. By simplifying

**26. In a first-order RL circuit, what component determines the time constant?**

- a) Resistor
- b) Capacitor
- c) Inductor
- d) Voltage Source

Answer: A. Resistor

**27. How do you calculate the time constant of a first-order RC circuit?**

- a)  $\tau = RC$
- b)  $\tau = LR$
- c)  $\tau = 1/L$
- d)  $\tau = 1/RC$

Answer: A.  $\tau = RC$

**28. What is the purpose of Norton's Theorem in circuit analysis?**

- a) To simplify
- b) To confuse
- c) To complicate
- d) To obfuscate

Answer: A. To simplify

**29. How is Superposition Theorem applied in circuit analysis?**

- a) By considering
- b) By ignoring
- c) By complicating
- d) By simplifying

Answer: B. By ignoring

**30. What is the primary objective of analyzing circuits using KCL and KVL?**

- a) To simplify
- b) To complicate

- c) To confuse
- d) To obfuscate

Answer: A. To simplify

**31. How do you calculate the equivalent resistance in a circuit using Thevenin's Theorem?**

- a) By shorting
- b) By opening
- c) By removing
- d) By replacing

Answer: B. By opening

**32. What is the significance of Norton's Theorem in circuit analysis?**

- a) It simplifies
- b) It complicates
- c) It confuses
- d) It obfuscates

Answer: A. It simplifies

**33. How do you determine the Thevenin equivalent voltage of a circuit?**

- a) By shorting
- b) By opening
- c) By removing
- d) By replacing

Answer: B. By opening

**34. What is the purpose of using Thevenin's Theorem in circuit analysis?**

- a) To simplify
- b) To complicate
- c) To confuse
- d) To obfuscate



Answer: A. To simplify

**35. How does Superposition Theorem simplify circuit analysis?**

- a) By considering
- b) By ignoring
- c) By complicating
- d) By simplifying

Answer: D. By simplifying

**36. In a first-order RL circuit, what component determines the time constant?**

- a) Resistor
- b) Capacitor
- c) Inductor
- d) Voltage Source

Answer: A. Resistor

**37. How do you calculate the time constant of a first-order RC circuit?**

- a)  $\tau = RC$
- b)  $\tau = LR$
- c)  $\tau = 1/L$
- d)  $\tau = 1/RC$

Answer: A.  $\tau = RC$

**38. What is the purpose of Norton's Theorem in circuit analysis?**

- a) To simplify
- b) To confuse
- c) To complicate
- d) To obfuscate

Answer: A. To simplify

**39. How is Superposition Theorem applied in circuit analysis?**

- a) By considering
- b) By ignoring
- c) By complicating
- d) By simplifying

Answer: B. By ignoring

**40. What is the primary objective of analyzing circuits using KCL and KVL?**

- a) To simplify
- b) To complicate
- c) To confuse
- d) To obfuscate

Answer: A. To simplify

**41. How do you calculate the equivalent resistance in a circuit using Thevenin's Theorem?**

- a) By shorting
- b) By opening
- c) By removing
- d) By replacing

Answer: B. By opening

**42. What is the significance of Norton's Theorem in circuit analysis?**

- a) It simplifies
- b) It complicates
- c) It confuses
- d) It obfuscates

Answer: A. It simplifies

**43. How do you determine the Thevenin equivalent voltage of a circuit?**

- a) By shorting
- b) By opening
- c) By removing
- d) By replacing

Answer: B. By opening

**44. What is the purpose of using Thevenin's Theorem in circuit analysis?**

- a) To simplify
- b) To complicate
- c) To confuse
- d) To obfuscate

Answer: A. To simplify

**45. How does Superposition Theorem simplify circuit analysis?**

- a) By considering
- b) By ignoring
- c) By complicating
- d) By simplifying

Answer: D. By simplifying

**46. In a first-order RL circuit, what component determines the time constant?**

- a) Resistor
- b) Capacitor
- c) Inductor
- d) Voltage Source

Answer: A. Resistor

**47. How do you calculate the time constant of a first-order RC circuit?**

- a)  $\tau = RC$
- b)  $\tau = LR$

c)  $\tau = 1/L$

d)  $\tau = 1/RC$

Answer: A.  $\tau = RC$

**48. What is the purpose of Norton's Theorem in circuit analysis?**

- a) To simplify
- b) To confuse
- c) To complicate
- d) To obfuscate

Answer: A. To simplify

**49. How is Superposition Theorem applied in circuit analysis?**

- a) By considering
- b) By ignoring
- c) By complicating
- d) By simplifying

Answer: B. By ignoring

**50. What is the primary objective of analyzing circuits using KCL and KVL?**

- a) To simplify
- b) To complicate
- c) To confuse
- d) To obfuscate

Answer: A. To simplify

**51. What is the phasor representation used for in AC circuits?**

- a) To represent voltage and current
- b) To represent resistance
- c) To represent power
- d) To represent frequency

Answer: A. To represent voltage and current

**52. What does the rms value of an AC waveform represent?**

- a) Average value
- b) Peak value
- c) Effective value
- d) Maximum value

Answer: C. Effective value

**53. What is the power factor of a purely resistive circuit?**

- a) 0
- b) 1
- c) -1
- d)  $\infty$

Answer: B. 1

**54. How is reactive power defined in AC circuits?**

- a) Power that performs useful work
- b) Power that doesn't perform work
- c) Power that is wasted
- d) Power that is constant

Answer: B. Power that doesn't perform work

**55. What is the main advantage of analyzing AC circuits using phasor representation?**

- a) Simplicity
- b) Accuracy
- c) Complexity reduction
- d) Increased computational load

Answer: A. Simplicity

**56. What is the resonance frequency of a series RLC circuit?**

- a)  $f = 1/(2\pi\sqrt{LC})$
- b)  $f = 1/(\pi\sqrt{LC})$
- c)  $f = 1/(4\pi\sqrt{LC})$
- d)  $f = 1/(8\pi\sqrt{LC})$

Answer: A.  $f = 1/(2\pi\sqrt{LC})$

**57. In a star (Y) connection of three-phase circuits, what is the relation between line and phase currents?**

- a) Line current = Phase current
- b) Line current > Phase current
- c) Line current < Phase current
- d) Line current has no relation to phase current

Answer: A. Line current = Phase current

**58. What happens to the impedance in a parallel RLC circuit when the frequency approaches resonance?**

- a) Impedance increases
- b) Impedance decreases
- c) Impedance remains constant
- d) Impedance becomes zero

Answer: B. Impedance decreases

**59. How does a delta ( $\Delta$ ) connection differ from a star (Y) connection in three-phase circuits?**

- a) Delta has a neutral wire
- b) Star has a neutral wire
- c) Delta lacks a neutral wire
- d) Star lacks a neutral wire

Answer: C. Delta lacks a neutral wire

**60. What is the primary reason for using three-phase circuits in industrial applications?**

- a) Efficiency
- b) Simplicity
- c) Cost-effectiveness
- d) Complexity

Answer: A. Efficiency

**61. How does a capacitor affect the power factor in an AC circuit?**

- a) Increases it
- b) Decreases it
- c) Does not affect it
- d) Depends on the capacitor value

Answer: A. Increases it

**62. What is the relationship between real power and apparent power in AC circuits?**

- a) Equal
- b) Real power > Apparent power
- c) Real power < Apparent power
- d) No relationship

Answer: A. Equal

**63. Which component dominates the impedance in an inductive circuit at high frequencies?**

- a) Capacitive reactance
- b) Inductive reactance
- c) Resistance
- d) Both inductive and capacitive reactance

Answer: C. Resistance

**64. What is the phase relationship between voltage and current in a purely capacitive circuit?**

- a) Voltage leads current
- b) Voltage lags current
- c) Voltage and current are in phase
- d) No relationship

Answer: A. Voltage leads current

**65. How does the power factor correction impact the efficiency of AC circuits?**

- a) Increases it
- b) Decreases it
- c) Does not affect it
- d) Depends on the load

Answer: A. Increases it

**66. What happens to the impedance of a series RLC circuit at resonance?**

- a) It increases
- b) It decreases
- c) It remains constant
- d) It becomes zero

Answer: D. It becomes zero

**67. In a three-phase balanced circuit, what is the relationship between line and phase voltages?**

- a) Line voltage = Phase voltage
- b) Line voltage > Phase voltage
- c) Line voltage < Phase voltage
- d) No relationship

Answer: A. Line voltage = Phase voltage

**68. What is the significance of power factor in AC circuits?**



- a) Indicates circuit efficiency
- b) Determines voltage levels
- c) Influences impedance
- d) Determines power generation

Answer: A. Indicates circuit efficiency

**69. How does a parallel RLC circuit behave at resonance?**

- a) Maximum current flows
- b) Minimum current flows
- c) Voltage drop is maximum
- d) Both voltage and current are minimum

Answer: A. Maximum current flows

**70. In a series RLC circuit, at resonance, what happens to the impedance?**

- a) It increases
- b) It decreases
- c) It remains constant
- d) It becomes infinite

Answer: B. It decreases

**71. How do you calculate the resonant frequency of an RLC circuit?**

- a)  $f = 1/(2\pi\sqrt{LC})$
- b)  $f = 1/(\pi\sqrt{LC})$
- c)  $f = 1/(4\pi\sqrt{LC})$
- d)  $f = 1/(8\pi\sqrt{LC})$

Answer: A.  $f = 1/(2\pi\sqrt{LC})$

**72. What is the effect of adding an inductor in series with a capacitor in a resonant circuit?**

- a) Decreases resonance frequency
- b) Increases resonance frequency

- c) No effect on resonance frequency
- d) Shifts resonance frequency

Answer: A. Decreases resonance frequency

**73. What happens to the impedance of a parallel RLC circuit when frequency increases beyond resonance?**

- a) It decreases
- b) It increases
- c) It remains constant
- d) It becomes infinite

Answer: B. It increases

**74. What is the effect of resistance in an RLC circuit at resonance?**

- a) Maximum power dissipation
- b) Minimum power dissipation
- c) No power dissipation
- d) Power dissipation is constant

Answer: B. Minimum power dissipation

**75. What is the purpose of power factor correction capacitors in AC circuits?**

- a) To increase voltage
- b) To decrease current
- c) To improve power factor
- d) To reduce power consumption

Answer: C. To improve power factor

**76. What is the significance of resonance in electrical circuits?**

- a) It minimizes power loss
- b) It maximizes power generation
- c) It optimizes power factor

d) It maximizes power transfer

Answer: D. It maximizes power transfer

**77. What happens to the voltage across a capacitor in an AC circuit as frequency increases?**

- a) It decreases
- b) It increases
- c) It remains constant
- d) It becomes zero

Answer: B. It increases

**78. What is the effect of adding a resistor in series with a capacitor in a resonant circuit?**

- a) Increases Q factor
- b) Decreases Q factor
- c) No effect on Q factor
- d) Shifts resonance frequency

Answer: B. Decreases Q factor

**79. How does the quality factor (Q) of a resonant circuit relate to bandwidth?**

- a) Inversely proportional
- b) Directly proportional
- c) No relationship
- d) Depends on frequency

Answer: A. Inversely proportional

**80. What is the effect of adding a resistor in parallel with an inductor in a resonant circuit?**

- a) Increases Q factor
- b) Decreases Q factor
- c) No effect on Q factor

d) Shifts resonance frequency

Answer: A. Increases Q factor

**81. What is the relationship between reactance and frequency in a capacitor?**

- a) Directly proportional
- b) Inversely proportional
- c) No relationship
- d) Depends on capacitance

Answer: A. Directly proportional

**82. How does a parallel RLC circuit behave at frequencies below resonance?**

- a) It behaves like an inductor
- b) It behaves like a capacitor
- c) It behaves like a resistor
- d) It behaves like an open circuit

Answer: B. It behaves like a capacitor

**83. What is the primary function of a capacitor in an AC circuit?**

- a) To store energy
- b) To limit current flow
- c) To increase resistance
- d) To convert AC to DC

Answer: A. To store energy

**84. What is the effect of adding an inductor in parallel with a capacitor in a resonant circuit?**

- a) Increases resonance frequency
- b) Decreases resonance frequency
- c) No effect on resonance frequency
- d) Shifts resonance frequency

Answer: B. Decreases resonance frequency

**85. How does a series RLC circuit behave at frequencies above resonance?**

- a) It behaves like an inductor
- b) It behaves like a capacitor
- c) It behaves like a resistor
- d) It behaves like an open circuit

Answer: A. It behaves like an inductor

**86. What is the effect of adding a capacitor in parallel with an inductor in a resonant circuit?**

- a) Increases resonance frequency
- b) Decreases resonance frequency
- c) No effect on resonance frequency
- d) Shifts resonance frequency

Answer: A. Increases resonance frequency

**87. What happens to the voltage across an inductor in an AC circuit as frequency increases?**

- a) It decreases
- b) It increases
- c) It remains constant
- d) It becomes zero

Answer: A. It decreases

**88. What is the relationship between current and frequency in an inductor?**

- a) Directly proportional
- b) Inversely proportional
- c) No relationship
- d) Depends on inductance

Answer: A. Directly proportional

**89. What is the function of a resistor in an AC circuit?**

- a) To store energy
- b) To limit current flow
- c) To generate electrical energy
- d) To produce magnetic field

Answer: B. To limit current flow

**90. What is the effect of adding a resistor in parallel with a capacitor in a resonant circuit?**

- a) Increases resonance frequency
- b) Decreases resonance frequency
- c) No effect on resonance frequency
- d) Shifts resonance frequency

Answer: B. Decreases resonance frequency

**91. How does the impedance of a series RLC circuit change with frequency?**

- a) It decreases
- b) It increases
- c) It remains constant
- d) It becomes infinite

Answer: B. It increases

**92. What is the primary function of an inductor in an AC circuit?**

- a) To store energy
- b) To limit current flow
- c) To generate electrical energy
- d) To produce magnetic field

Answer: D. To produce magnetic field

**93. What is the phase relationship between voltage and current in a purely inductive circuit?**

- a) Voltage leads current
- b) Voltage lags current
- c) Voltage and current are in phase
- d) No relationship

Answer: B. Voltage lags current

**94. How does the addition of an inductor affect the resonance frequency in a resonant circuit?**

- a) Increases it
- b) Decreases it
- c) No effect
- d) Depends on inductor value

Answer: A. Increases it

**95. What is the effect of adding a capacitor in series with an inductor in a resonant circuit?**

- a) Increases resonance frequency
- b) Decreases resonance frequency
- c) No effect on resonance frequency
- d) Shifts resonance frequency

Answer: B. Decreases resonance frequency

**96. What is the relationship between voltage and frequency in a capacitor?**

- a) Directly proportional
- b) Inversely proportional
- c) No relationship
- d) Depends on capacitance

Answer: B. Inversely proportional

**97. What is the effect of adding a resistor in series with an inductor in a resonant circuit?**

- a) Increases resonance frequency
- b) Decreases resonance frequency
- c) No effect on resonance frequency
- d) Shifts resonance frequency

Answer: B. Decreases resonance frequency

**98. How does the impedance of a capacitor change with frequency in an AC circuit?**

- a) It increases
- b) It decreases
- c) It remains constant
- d) It becomes infinite

Answer: A. It increases

**99. What is the relationship between current and frequency in a capacitor?**

- a) Directly proportional
- b) Inversely proportional
- c) No relationship
- d) Depends on capacitance

Answer: B. Inversely proportional

**100. What is the primary function of a capacitor in an AC circuit?**

- a) To store energy
- b) To limit current flow
- c) To generate electrical energy
- d) To produce magnetic field

Answer: A. To store energy

**101. What is the purpose of an ideal transformer?**



- a) To step up voltage
- b) To step down voltage
- c) To maintain voltage
- d) To regulate voltage

Answer: B. To step down voltage

**102. Which losses are present in practical transformers?**

- a) Copper losses
- b) Hysteresis losses
- c) Leakage flux losses
- d) All of the above

Answer: D. All of the above

**103. What is meant by regulation in transformers?**

- a) The ability to maintain voltage
- b) The ability to change voltage
- c) The ability to withstand voltage
- d) The ability to measure voltage

Answer: A. The ability to maintain voltage

**104. Which factor affects the efficiency of a transformer?**

- a) Load current
- b) Frequency
- c) Both load current and frequency
- d) Voltage

Answer: C. Both load current and frequency

**105. What is the primary function of an auto-transformer?**

- a) To provide voltage transformation
- b) To increase efficiency
- c) To regulate voltage

d) To decrease size

Answer: A. To provide voltage transformation

**106. What are the advantages of auto-transformers over traditional transformers?**

- a) Lower cost
- b) Reduced weight
- c) Both lower cost and reduced weight
- d) Better efficiency

Answer: C. Both lower cost and reduced weight

**107. What are the disadvantages of auto-transformers?**

- a) Lack of isolation
- b) Higher cost
- c) Both lack of isolation and higher cost
- d) Reduced efficiency

Answer: A. Lack of isolation

**108. Which connection of three-phase transformers offers better voltage regulation?**

- a) Star-star (Y-Y) connection
- b) Delta-delta ( $\Delta$ - $\Delta$ ) connection
- c) Delta-star ( $\Delta$ -Y) connection
- d) Star-delta (Y- $\Delta$ ) connection

Answer: A. Star-star (Y-Y) connection

**109. What does the delta-delta ( $\Delta$ - $\Delta$ ) connection offer in terms of performance?**

- a) High fault tolerance
- b) Better voltage regulation
- c) Neutral connection
- d) Lower line currents

Answer: A. High fault tolerance

**110. Which connection configuration is suitable for applications requiring a neutral point for grounding and providing single-phase loads?**

- a) Star-star (Y-Y) connection
- b) Delta-delta ( $\Delta$ - $\Delta$ ) connection
- c) Delta-star ( $\Delta$ -Y) connection
- d) Star-delta (Y- $\Delta$ ) connection

Answer: A. Star-star (Y-Y) connection

**111. What is the primary advantage of the delta-star ( $\Delta$ -Y) transformer connection?**

- a) High fault tolerance
- b) Better voltage regulation
- c) Absence of neutral connection
- d) Higher impedance

Answer: C. Absence of neutral connection

**112. Which connection configuration offers better performance in terms of fault tolerance and unbalanced loads?**

- a) Delta-star ( $\Delta$ -Y) connection
- b) Delta-delta ( $\Delta$ - $\Delta$ ) connection
- c) Star-star (Y-Y) connection
- d) Star-delta (Y- $\Delta$ ) connection

Answer: A. Delta-star ( $\Delta$ -Y) connection

**113. What is the main limitation of the star-delta (Y- $\Delta$ ) transformer connection?**

- a) Absence of a neutral point
- b) Higher voltage regulation
- c) Lower fault tolerance
- d) Better efficiency

Answer: A. Absence of a neutral point

**114. Which parameter indicates how well a transformer maintains voltage under varying load conditions?**

- a) Regulation
- b) Efficiency
- c) Impedance
- d) Power factor

Answer: A. Regulation

**115. What is the measure of how effectively a transformer converts input power into output power?**

- a) Efficiency
- b) Regulation
- c) Impedance
- d) Power factor

Answer: A. Efficiency

**116. What are the primary losses in transformers that affect their efficiency?**

- a) Copper losses
- b) Core losses
- c) Both copper losses and core losses
- d) Stray losses

Answer: C. Both copper losses and core losses

**117. Which type of transformer connection is more suitable for industrial motor drives and variable frequency drives?**

- a) Star-delta (Y- $\Delta$ ) connection
- b) Delta-delta ( $\Delta$ - $\Delta$ ) connection
- c) Delta-star ( $\Delta$ -Y) connection
- d) Star-star (Y-Y) connection

Answer: A. Star-delta (Y- $\Delta$ ) connection

**118. What is the primary advantage of an auto-transformer compared to traditional transformers?**

- a) Compact size
- b) Lower cost
- c) Better efficiency
- d) Higher isolation

Answer: A. Compact size

**119. What is the role of regulation in transformers?**

- a) To maintain voltage
- b) To regulate current
- c) To reduce losses
- d) To enhance efficiency

Answer: A. To maintain voltage

**120. What does efficiency measure in a transformer?**

- a) How well it converts input power
- b) How well it regulates voltage
- c) How well it maintains current
- d) How well it reduces losses

Answer: A. How well it converts input power

**121. Which losses contribute to decreased efficiency in transformers?**

- a) Copper and core losses
- b) Hysteresis and eddy current losses
- c) Leakage and stray losses
- d) All of the above

Answer: D. All of the above

**122. What is the primary function of an auto-transformer?**

- a) To provide voltage transformation
- b) To increase efficiency
- c) To regulate voltage
- d) To decrease size

Answer: A. To provide voltage transformation

**123. Which connection of three-phase transformers offers better voltage regulation?**

- a) Star-star (Y-Y) connection
- b) Delta-delta ( $\Delta$ - $\Delta$ ) connection
- c) Delta-star ( $\Delta$ -Y) connection
- d) Star-delta (Y- $\Delta$ ) connection

Answer: A. Star-star (Y-Y) connection

**124. What is the primary advantage of the delta-star ( $\Delta$ -Y) transformer connection?**

- a) High fault tolerance
- b) Better voltage regulation
- c) Absence of neutral connection
- d) Higher impedance

Answer: C. Absence of neutral connection

**125. Which parameter indicates how well a transformer maintains voltage under varying load conditions?**

- a) Regulation
- b) Efficiency
- c) Impedance
- d) Power factor

Answer: A. Regulation